

CONTENTS

PREFACE	ix
ABOUT THE AUTHORS	xi
LIST OF ELECTRICAL CONSTANTS	xiii
CHAPTER 1: FUNDAMENTALS OF SEMICONDUCTOR ELECTRONICS	1
1.1 Introduction	1
1.2 Electrons in Atoms	2
1.3 Electrons in Solids	5
1.4 The Structure of Energy Bands For Insulators, Semiconductors And Metals	6
1.5 Covalent Bond in Semiconductors	7
1.6 Formation of Holes in Semiconductors	8
1.7 Intrinsic and Extrinsic Semiconductors	9
1.8 Density of Charge	11
1.9 Dependence of n_i with Temperature T	12
1.10 Conduction in Semiconductor Materials	13
1.11 Chapter Summary	17
PROBLEMS AND SOLUTIONS	19
CHAPTER 2: P – N JUNCTION DIODES	25
2.1 Introduction	25
2.2 Open Circuit Diodes	26
2.3 Forward Biased Diodes	27
2.4 Reverse Biased Diode	28

2.5	Current – Voltage (I – V) Characteristics of Diodes	29
2.6	Diodes Resistances	30
2.7	The Use of Heat Sink in Diode Circuit	31
2.8	Breakdown Diodes	33
2.9	Zener Diode as Voltage Regulators	34
2.10	Chapter Summary	35
	PROBLEMS AND SOLUTIONS	36

CHAPTER 3: DIODE AS A CIRCUIT ELEMENT 41

3.1	Introduction	41
3.2	Load Line and Operating Point Concepts	42
3.3	Half Wave Rectifier	43
3.4	Full Wave Rectifier	46
3.5	Filter Circuit	48
3.6	Clipping Circuit	52
3.7	Clamping Circuit	53
3.8	Chapter Summary	54
	PROBLEMS AND SOLUTIONS	55

CHAPTER 4: OPERATION AND BIASING OF BIPOLAR TRANSISTORS 65

4.1	Introduction	65
4.2	Open Circuit Transistor	66
4.3	Transistor Biased In the Active (Linear) Region	67
4.4	Transistor Configuration in Amplifier Application	70
4.5	Common Base Configuration	71
4.6	Common Base Input Characteristics	72
4.7	Common Base Output	73
4.8	Relationship Between Output Current I_c and Input Current I_E	74
4.9	Common Emitter Configuration	75

4.10 Relation Between Output Current and Output Voltage	76
4.11 Common Collector Configuration	78
4.12 Biasing Of a Simple Transistor Amplifier	78
4.13 Fixed Biasing	81
4.14 Self Biasing	82
4.15 Analysis of Self Bias Circuit	82
4.16 Voltage Feedback Bias	84
4.17 Common Collector Bias Circuit (Emitter Follower)	85
4.18 Design of Direct Current Bias Circuit	87
4.19 Chapter Summary	90
PROBLEMS AND SOLUTIONS	91

CHAPTER 5: FIELD EFFECT TRANSISTOR 99

5.1 Introduction	99
5.2 Structure of JFET	99
5.3 Characteristics of JFET	101
5.4 JFET Parameters	103
5.5 Structure and Characteristics Of MOSFET	104
5.6 Biasing Circuit of JFET	107
5.7 Biasing Circuit for Depletion Mode MOSFET Transistor	112
5.8 Chapter Summary	112
PROBLEMS AND SOLUTIONS	113

CHAPTER 6: ANALYSIS OF BIPOLAR TRANSISTORS AT LOW FREQUENCY 127

6.1 Introduction	127
6.2 The h – Parameter Hybrid Model	128
6.3 Analysis of Amplifier Circuit Using H- Parameter Model	131
6.4 Taking into Account Resistances R_S and R_B	135

6.5 Taking into Account R_1 , R_2 at Input and R_C at Output	137
6.6 Emitter Follower Configuration	139
6.7 Chapter Summary	141
PROBLEMS AND SOLUTIONS	142
CHAPTER 7: ANALYSIS OF JFET AT LOW FREQUENCY	153
7.1 Introduction	153
7.2 JFET Small Signal Model	154
7.3 Common Source Amplifier Model	156
7.4 Amplifier with Non Bypassed Resistance	158
7.5 The Effect of Load Resistance	160
7.6 The Effect of Input Source Resistance	161
7.7 Source Follower Circuit (Common Drain)	162
7.8 Approximate Model for JFET	164
7.9 Chapter Summary	165
PROBLEMS AND SOLUTIONS	166
CHAPTER 8: INTEGRATED CIRCUIT	177
8.1 Introduction	177
8.2 The Latest Development	179
8.3 Fabrication of Monolithic ICs	180
8.4 Thick and Thin Films ICs	186
8.5 Hybrid ICs	187
8.6 Chapter Summary	188
PROBLEMS AND SOLUTIONS	189
REFERENCES	198
INDEX	200